

Course name: Digital Design

Number: CS 223

Section: 3


Number of the lab: 2

Your name: Ahmet Faruk Ulutaş


Student ID: 21803717

Date: 23.02.2021

B) Schematic for a 1-bit fulladder

 

 C) Schematic for a 2-bit adder made from two 1-bit fulladders



D) Dataflow Systemverilog module for the 1-bit fulladder

```
module dataflow( input logic x, y, cin, output logic sum, cout);
```

```
    assign sum = (x ^ y) ^ cin;
```

```
    assign cout = (x & y) | ((x ^ y) & cin);
```

```
endmodule
```

E) Structural Systemverilog module for the 1-bit fulladder

```
module structuralOneBitFullAdder( input x, y, cin, output sum, cout );
```

```
    logic out0, out1, out2;
```

```
    xor0 xor0(x, y, out0);
```

```
    xor0 xor1(out0, cin, sum);
```

```
    and0 and0(x, y, out1);
```

```
    and0 and1(out0, cin, out2);
```

```
    or0 or0(out2, out1, cout);
```

```
endmodule
```

```
module xor0( input a, b, output out);
```

```
    assign out = a ^ b;
```

```
endmodule
```

```
module and0( input a, b, output out);
```

```
    assign out = a & b;
```

```
endmodule
```

```
module or0( input a, b, output out);
```

```
    assign out = a | b;
```

```
endmodule
```

TESTBENCH

```
module testbenchOneBitFullAdder();
```

```
    logic x, y, cin, sum, cout;
```

```
    structuralOneBitFullAdder dut( x, y, cin, sum, cout);
```

```

initial begin
    x = 0; y = 0; cin = 0; #10;
    cin = 1; #10;
    y = 1; cin = 0; #10;
    cin = 1; #10;
    x = 1; y = 0; cin = 0; #10;
    cin = 1; #10;
    y = 1; cin = 0; #10;
    cin = 1; #10;
end

```

```

endmodule

```

F) Structural Systemverilog module for the 2-bit adder

```

module structuralTwoBitAdder( input logic a0, b0, cin, a1, b1, output logic s0, s1, cout1);

    logic cout0;

    fullAdder fullAdder0( a0, b0, cin, s0, cout0);
    fullAdder fullAdder1( a1, b1, cout0, s1, cout1);

endmodule

```

```

module fullAdder( input logic a, b, cin, output logic s, cout);

    logic out0, out1, out2;

    assign out0 = a ^ b;
    assign s = out0 ^ cin;
    assign out1 = a & b;

```

```
assign out2 = out0 & cin;  
assign cout = out2 | out1;
```

```
Endmodule
```

```
TESTBENCH
```

```
module testbenchTwoBitAdder();
```

```
logic a0, b0, cin, a1, b1, s0, s1, cout1;
```

```
structuralTwoBitAdder dut( a0, b0, cin, a1, b1, s0, s1, cout1);
```

```
initial begin
```

```
    a0 = 0; b0 = 0; cin = 0; a1 = 0; b1 = 0; #10;
```

```
    b1 = 1; #10;
```

```
    a1 = 1; b1 = 0; #10;
```

```
    b1 = 1; #10;
```

```
    cin = 1; a1 = 0; b1 = 0; #10;
```

```
    b1 = 1; #10;
```

```
    a1 = 1; b1 = 0; #10;
```

```
    b1 = 1; #10;
```

```
    b0 = 1; cin = 0; a1 = 0; b1 = 0; #10;
```

```
    b1 = 1; #10;
```

```
    a1 = 1; b1 = 0; #10;
```

```
    b1 = 1; #10;
```

```
    cin = 1; a1 = 0; b1 = 0; #10;
```

```
    b1 = 1; #10;
```

```
    a1 = 1; b1 = 0; #10;
```

```
    b1 = 1; #10;
```

```
    a0 = 1; b0 = 0; cin = 0; a1 = 0; b1 = 0; #10;
```

```
b1 = 1; #10;  
a1 = 1; b1 = 0; #10;  
b1 = 1; #10;  
cin = 1; a1 = 0; b1 = 0; #10;  
b1 = 1; #10;  
a1 = 1; b1 = 0; #10;  
b1 = 1; #10;  
b0 = 1; cin = 0; a1 = 0; b1 = 0; #10;  
b1 = 1; #10;  
a1 = 1; b1 = 0; #10;  
b1 = 1; #10;  
cin = 1; a1 = 0; b1 = 0; #10;  
b1 = 1; #10;  
a1 = 1; b1 = 0; #10;  
b1 = 1; #10;
```

end

endmodule